

Application Note

Single Input to Differential Input

AKM codecs, DACs and ADCs have either single-ended (unbalanced) or differential (balanced) inputs. If your design calls for converting a single-ended input to a differential input, please consider using the following circuit.

